

18-447 Synthesizable Verilog Tutorial


Peter Milder
Dept of ECE, CMU
January 21, 2009

Announcements: none

Handouts: Verilog Tutorial

RTL Verilog Review (The 447 Subset)

Schematic Capture

 


Hardware Description Language

```
always @ (posedge Clk) begin
    if (a >= b) begin
        a <= a - b;
        b <= b;
    end else begin
        a <= b;
        b <= a;
    end
end
```


RT-Level Descriptions

- ◆ Textual descriptions of logic circuits
 - different **representation**, but essentially the same **semantics/abstraction** as in schematic capture

So why is it any better?
- ◆ Fine-grain behavior: synchronous **register transfer**
 - a collection of **synchronous_state** elements (e.g. registers)
 - a collection of **combinational** logic that computes the next-state (NS or Q') values of state elements based current-state (CS or Q) values of state elements
 - all state elements take on new values simultaneously (implies a globally synchronous clock)

 

RTL Execution/Timing

 


Verilog Modules

- ◆ A module with input and output ports

```
module ff_en( input Din, En, CLK,
              output Dout );
```

... body of module ...

```
endmodule
```

 


You are NOT writing a Verilog “program”.

You are describing hardware in text

Hierarchical Descriptions

 - ◆ Coarse-grain structure
 - A hierarchy of modules
 - A module contains RTL logic and/or, recursively, a network of modules interconnected by wires
 - A module is a **convenience**
 - a design encapsulation/abstraction
 - partitions a design into manageable chunks (vertically and horizontally)
 - reusable design
- ◆ How is a hardware module different from a software function?




Module Instantiation and Hierarchy

```
module shift_reg (input Din, En, CLK,
                  output Dout );
  wire n1;

  ff_en ff1 (.Din ( Din ),
              .En ( En ),
              .CLK ( CLK ),
              .Dout ( n1 ));

   ff_en ff2 (.Din ( n1 ),
              .En ( En ),
              .CLK ( CLK ),
              .Dout ( Dout ));
endmodule
```



Use **named notation** to wire modules:
More likely to get port hookups right!
E.g., connect **ff1**'s **Dout** to wire **n1**, ...

Parameters

- ◆ Can parameterize modules:

```
module pmod #(parameter width = 4)
  (input [width-1:0] in,
   output [width-1:0] out);

endmodule
```

default parameter value

```
width = 4 → module topmod( ... );
width = 5 →   pmod                      m0(.in(a), .out(b));
width = 6 →   pmod #(5)                  m1(.in(c), .out(d));
               pmod #(.width(6)) m2(.in(e), .out(f));
endmodule
```

Arrays of Modules

- ◆ Hardware frequently has many arrays
 - Verilog distributes **some** connections across arrays for you
 - 1D arrays only
 - Multi-dimensional arrays can be emulated with “hacks”

```

module big_reg #(parameter width = 4)
  (input [width:0] Din,
   input En, CLK,
   output [width:0] Dout );
  wire [width:0] n1;
  ff_en ff[width:0] ( .Din ( Din ),
                      .En ( En ),
                      .CLK ( CLK ),
                      .Dout ( n1 ));
endmodule

```

Arrays of modules just like wires

Automatically distributes multi-bit and single-bit inputs (if sizes match)

Combinational Logic


Wires, expressions and assign

```

module ff_en (input Din, En, CLK,
              output Dout);
  wire cs, ns;
  assign Dout = cs;
  assign ns = En ? Din : cs;
  ff ff1 ( .Din ( ns ),
            .CLK ( CLK ),
            .Dout ( cs ) );
endmodule

```

 continuous assignment:
bind wire to an “expression”



Synchronous Sequential Logic

```

module ff (input Din, CLK,
           output Dout);
  reg q;
  assign Dout = q ;
endmodule


```

"reg" declares a "stateful" variable
 (as opposed to a stateless wire);
 reg does not declare a "register"

trigger list
 always @ (posedge CLK) begin
 q <= Din ;
 end

trigger event
 delayed assignment symbol

an "always" block (aka process)

 

Din → **ff** → **Dout**
CLK

A reg variable should only be assigned in *at most one* "always" block!!

Combinational Logic

Procedural Assignment

```

module ff_en (input Din, En, CLK
               output Dout);
  wire cs;
  reg ns;
  assign Dout = cs;
  always @ ( Din or cs or En ) begin
    if (En) begin
      ns = Din;
    end else begin
      ns = cs;
    end
  end
  ff ff1 (.Din ( ns ),
           .CLK ( CLK ),
           .Dout ( cs ));
endmodule

```


this "reg" is a
 combinational value

trigger list
 (must list **all** RHS vars.)
 (now, can use always @*)

describing combinational logic as
 a sequential program (i.e. how to
 compute ns based on Din or En).

procedure assignment: ns retains the **last**
 assigned value at the end of the "always"

 A reg variable should appear on LHS in **at most one**
 always block!! A LHS reg must be assigned **at least**
 once following all possible control paths in a
 combinational block!!



Din → **OR** → **cs** → **ff** → **Dout**
En → **OR**
CLK

Combinational Logic

Procedural Assignments Gone Bad

```
module ff_en (input Din, En, CLK,
               output Dout);


    wire   cs;
    reg    ns;

    assign Dout = cs;

    always @ ( Din or cs or En ) begin
        if (En) begin
            ns = Din;
        end // else begin
        // ns = cs;
        // end
    end

    ff ff1 (.Din ( ns ),
             .CLK ( CLK ),
             .Dout ( cs ));

endmodule
```

 

What is missing?

Is this still combinational?

What will the synthesis tool
do with this?

Combinational Logic

Procedural Assignments Gone Bad

OK??

```
module ff_en (input Din, En, CLK,
               output Dout);


    wire   cs;
    reg    ns;

    assign Dout = cs ;

    always @ ( Din or cs or En ) begin
        ns = cs;
        if ( En ) begin
            ns = Din;
        end
    end

    ff ff1 (.Din ( ns ),
             .CLK ( CLK ),
             .Dout ( cs ));

endmodule
```

 

If there is control flow, always begin by providing a default assignment to each assigned LHS. Make it a habit.

Combinational Logic

Procedural Assignments Gone Bad

```
module ff_en (input Din, En, CLK,
              output Dout);

    wire    cs;
    reg     ns;


    assign Dout = cs;

    always @ ( Din or cs /* or En */ )
    begin
        ns = cs ;

        if ( En ) begin
            ns = Din;
        end
    end

    ff ff1 (.Din ( ns ),
             .CLK ( CLK ),
             .Dout ( cs ));

endmodule
```

 

Incomplete sensitivity lists
considered harmful!

What happens here?

Combinational Logic

Procedural Assignments Gone Bad

```
module ff_en (input Din, En, CLK
              output Dout);

    wire    cs;
    reg     ns;


    assign Dout = cs;

    always @ ( Din or cs or En )
    begin
        ns <= cs;

        if ( En )begin
            ns <= Din;
        end
    end

    ff ff1 (.Din ( ns ),
             .CLK ( CLK ),
             .Dout ( cs ));

endmodule
```

 

What is the value of ns here?

Combining Combinational and Sequential Logic

```
module ff_en (input Din, En, CLK
               output Dout);


    reg    Dout;      // sequential
    reg    Dout_next; // combinational

    always @ ( Din or Dout or En ) begin
        if ( En ) begin
            Dout_next = Din;
        end else begin
            Dout_next = Dout;
        end
    end

    always @ ( posedge CLK ) begin
        Dout <= Dout_next;
    end
endmodule
```

Never do

 - an always block that has **both** delayed and procedural assigns!!
- a reg assigned to by **both** delayed and procedural assigns!!



clearly combinational

clearly synch. sequential

Synthesis: under the hood

Inferring Synch Sequential Logic

```
always @ ( posedge CLK ) begin
    LHS <= F( RHS ) ;
end
```

- ◆ Edge triggered “always” block with delayed assignments
 - LHS are reg type and cannot be assigned by another always block
 - RHS are either reg or wire type, can overlap with LHS
 - always block can contain control flow---0 or 1 assign per LHS
- ◆ A register of the appropriate width is instantiated for every LHS reg variable
- ◆ The next-state value on the next clock edge is a combinational function of the RHS variables


Note: the RHS vars could be combinational or synchronous

Register Inference

```
reg [7:0]      count;
reg          and_bits,
            or_bits,
            xor_bits;

always @ (posedge CLK) begin
    if (reset)
        count <= 0;
    else
        count <= count + 1;

    and_bits <= &count;
    or_bits  <= |count;
    xor_bits <= ^count;
end
```

 

Register Inference + Retiming

```

reg [7:0]      count;
reg          and_bits,
            or_bits,
            xor_bits;

always @ (posedge CLK) begin
    if (reset)
        count <= 0;
    else
        count <= count + 1;

    and_bits <= &count;
    or_bits <= |count;
    xor_bits <= ^count;
end

```

```

reg [7:0]      count;
reg          and_bits,
            or_bits,
            xor_bits;

always @ (posedge CLK) begin
    if (reset)
        count <= 0;
    else
        count <= count + 1;
end

always @ (count) begin
    and_bits = &count;
    or_bits = |count;
    xor_bits = ^count;
end

```




Inferring Combinational Logic

- ◆ Continuous assignments: bind an expression to a wire
 - ◆ Always blocks:
 - procedural assignments to reg-type LHS
 - all input signals are included in the trigger list
⇒ LHS recomputed whenever inputs change
 - { LHS } does not intersect { inputs }
⇒ no feedback cycles
 - all LHS are assigned on all possible control paths
⇒ LHS does not depend on itself ⇒ no storage
- ⇒ A combinational relationship between RHS and LHS

Procedural Descriptions

 
```
{
  x = b;
  if (y)
    x = x + a;
}
```



```
{
  x1 = b;
  if (y)
    x2 = x1 + a;
  else
    x2 = x1
  ...
  x = xmax
}
```

to flatten out a procedural
description, convert to
single-assignment
 
```
{
  if (y)
    x = b + a;
  else
    x = b;
}
```



Sequentialized Description


```
output [15:0] z;
reg [15:0] z;

input [15:0] A;
input [15:0] B;

integer i;

always @ (A or B) begin
  z=0;

   for(i=0;i<=15;i=i+1) begin
    if (A[i]) begin
      z=z+(B<<i);
    end
  end
end
```



Try writing *that* in a continuous
assignment expression

Synthesizable Loops

- ◆ Static loops are allowed
 - good for scanning across fixed size vectors and arrays
- ◆ A loop must be statically unrollable, i.e.,
 - loop index must be integer type
 - loop index initial value must statically resolve to a constant
 - valid loop index operations are +, -
 - the valid loop condition test must test against a static limit using relational operators: <, <=, >, >=

Some tools even support bounded-recursive functions. We do not suggest this in 18-447.


Combinational Logic

- ◆ In general
 - RTL Synthesis tools let you control the combinational logic by the structure of your expressions
 - With optimizations turned off, tools translate an expression literally and faithfully
 - Most optimizations are turned-off by default
 - RTL Synthesis tools can infer “custom-width” {adders, subtractors, comparators}, multipliers and multiplexers, everything else is mapped as random logic
 - Simple syntax-directed translation
 - You can instantiate library modules explicitly to improve performance
 - Tool- and target-specific “pragmas” or “directives” permit fine-tuning.

Simple Example

- ◆ The statement
 
```
if (b < 10)
    y = a + b;
else
    y = a + 10;
```



- ◆ Maps to

- A comparator that compares the value of **b** with **10**
- An adder that has **a** and **b** as inputs
- An adder that has **a** and **10** as inputs
- A multiplexer (implied by the **if** statement) that controls the final value of **y**

- ◆ The width of the datapath depends type of **a**, **b** and **y**

Case-Switch

```
output [7:0] out;
input [2:0] in;
reg [7:0] out;

always @( in ) begin
    case (in)
        3'h0: out=1;
        3'h1: out=2;
        3'h2: out=4;
        3'h3: out=8;
        3'h4: out=16;
        3'h5: out=32;
        default: out=x;
    endcase
end
```

Watch out: keywords different from C/C++

Tells synthesis that everything else is don't care!

Verilog Compiler Directives

- ◆ Insert external file
 - `include "filename.v"
 - inserts filename.v at that line
 - ◆ Macros
 - `define MACRONAME value
 - Replace `MACRONAME with value everywhere in code
 - ◆ Macro-controlled conditionals
 - Use different code depending on which macros are defined


```
`ifdef SYNTHESIZE
`include "something_synthesizable.v"
`else
`include "something_not_synthesizable.v"
`endif
```
 - Also: `ifndef "if not defined"
- Don't forget
the backticks!**

Default Net Type

- ◆ By default, most tools will assume that undeclared values are 1-bit wires
- ◆ Instead, you can turn this “feature” off!

Before

```
module test (input [3:0] a,
             output [3:0] b);
    wire [3:0] typo;
    assign typo = a;
    assign b = typo;
endmodule
```

Assumes “typo” is a one-bit wire
(and doesn’t tell you!)

After

```
`default_nettype none

module test (input wire [3:0] a,
             output wire [3:0] b);
    wire [3:0] typo;
    assign typo = a;
    assign b = typo;
endmodule
```

Now need to explicitly declare inputs and outputs as “wires”

Gives error: “typo” undeclared

Readings

- ◆ Highly recommended readings,
 - HDL Compiler for Verilog: Reference Manual, Synopsys Documentation
 - Guide to HDL Coding Styles for Synthesis, Synopsys Documentation