

18-100 Lecture 22: Implementing Combinational Logic

James C. Hoe
Dept of ECE, CMU
April 9, 2015

Today's Goal: Design some combinational logic circuits


Announcements: Read Rizzoni 12.4 and 12.5

HW 8 due today

Handouts: Lab 11 for week of 4/20 (on Blackboard)
HW 9 due Tuesday 4/21 (on Blackboard)
HW 8 Solutions (on Blackboard later today)

Universality of NAND and NOR Gates

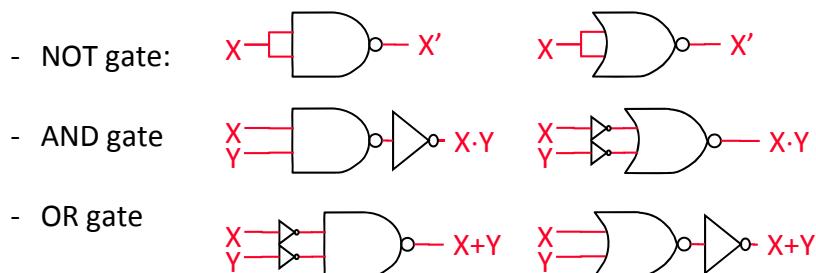- ◆ Either NAND or NOR is sufficient to implement AND/OR/NOT
 - convenient because inverting logic gates arise naturally in transistor-based implementations



- ◆ But still, how do we know AND/OR/NOT is sufficient to implement any combinational function imaginable?

Let's Design Something

- ◆ Input: 1-bit **A**, 1-bit **B**, and 1-bit **C**
- ◆ Output: 2-bit **S** that is a 2-bit unsigned integer;
indicates how many bits of the input **A**, **B** and **C** are asserted; possible values are 0, 1, 2, 3

- ◆ Start with the Truth Table

- 2^N rows for a function of N inputs
- better to enumerate input patterns systematically, e.g., as if counting
- uniquely and unambiguously define a combinational function

Now what?

A	B	C	S[1]	S[0]
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Canonical Sum-of-Products (SOP)

- ◆ Each row of a truth table corresponds to a distinct input combination (aka, a "minterm")

- e.g., row 0 corresponds to $A' \cdot B' \cdot C'$, aka m_0
- row 1 corresponds to $A' \cdot B' \cdot C$, aka m_1
- row 2 corresponds to $A' \cdot B \cdot C'$, aka m_2
- etc.

- ◆ Construct a function by OR'ing the minterms in the "on-set" (i.e., the 1s)

$$S[0] = A'B'C + A'BC' + AB'C' + ABC$$

m₁ m₂ m₄ m₇


$$S[1] = A'BC + AB'C + ABC' + ABC$$

m₃ m₅ m₆ m₇

A	B	C	S[1]	S[0]
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

2-level SOP Implementation

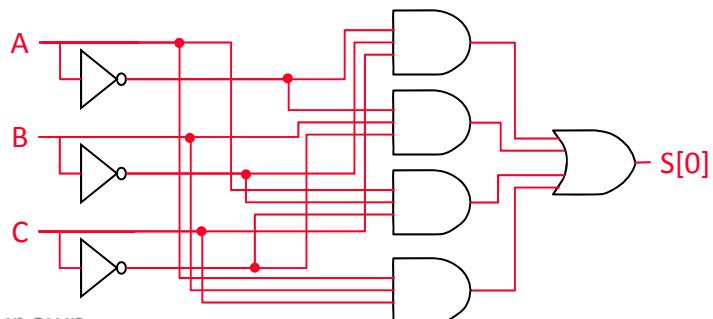
- ◆ $S[0] = A'B'C + A'BC' + AB'C' + ABC$
 - each minterm is a “product” (AND is boolean multiply)
 - $S[0]$ is the sum of products (OR is boolean addition)
- ◆ Every function has a truth table; every truth table has a corresponding “canonical” SOP form
 ⇒ every fxn can be implemented using AND/OR/NOT



Try S[1] on your own

NAND-NAND is SOP

- ◆ What if you have only NANDs

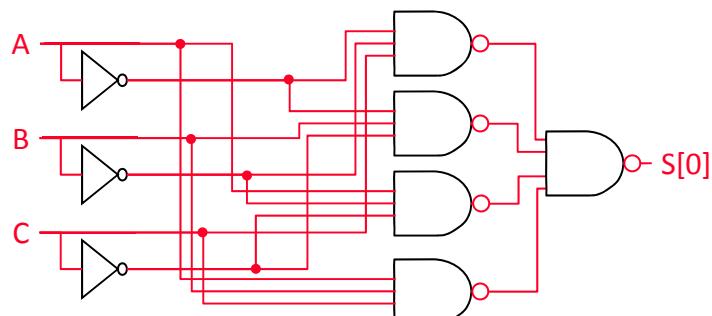

Canonical Product of Sums (POS)

- ◆ What if the truth table is mostly 1s and you are too lazy to write out all those minterms?

ANS: write SOP for F'

- ◆ E.g., $F' = A'B'C' + AB'C$

- ◆ Apply De Morgan to get back F in POS form


$$F = (A+B+C)(A'+B+C')$$

This is a maxterm, that is, $(A+B+C)$ is true everywhere except $A'B'C'$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

2-level POS Implementation

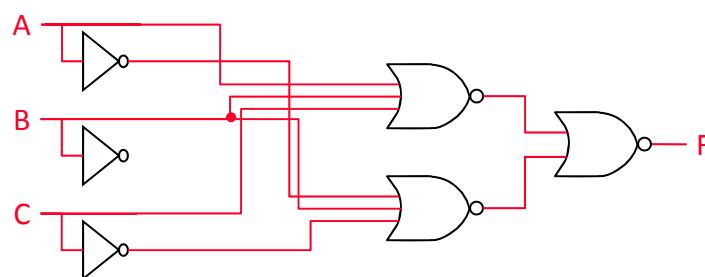- ◆ $F = (A+B+C)(A'+B+C')$
 - each maxterm is a “sum” (OR is boolean addition)
 - F is the product of sums (AND is boolean multiply)
- ◆ Every function also has a “canonical” POS form
- ◆ NOR-NOR is POS



Minimum SOP Form

- ◆ Simplified SOP expression that minimizes the number of gates and the number of input to gates, e.g.,

- ◆ $F = A'B'C + A'BC + AB'C + ABC' + ABC$
 $= A'B'C + A'BC + AB'C + ABC' + ABC + ABC$ rule 3
 $= A'B'C + A'BC + AB'C + ABC + ABC' + ABC$ rule 10
 $= A'B'C + A'BC + AB'C + ABC + AB(C' + C)$ rule 14
 $= A'B'C + A'BC + AB'C + ABC + AB \cdot 1$ rule 4
 $= A'B'C + A'BC + AB'C + ABC + AB$ rule 6

- ◆ Let's make the last 3 steps into a theorem

$$XY' + XY = X(Y' + Y) = X \cdot 1 = X \quad (\text{Uniting Theorem})$$

- ◆ $F = (A'B'C + A'BC) + (AB'C + ABC) + AB$
 $= A'C + AC + AB$
 $= C + AB$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Can we do any better? If not, can we know for sure?

Applying the Uniting Theorem

- ◆ How to recognize opportunities to “unite”?

- looking for pairs of minterms in the on-set that are distance-1 (reachable by toggling one input)

- ◆ E.g., ABC' and ABC



- F asserted if AB , independent of C
- replace $ABC' + ABC$ by AB in SOP

- ◆ But this is tricky to do . . .

- not all minterm neighbors are easy to see in a truth table
- united terms themselves can be further united, e.g., $A'C + AC = C$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth Table on a Cube

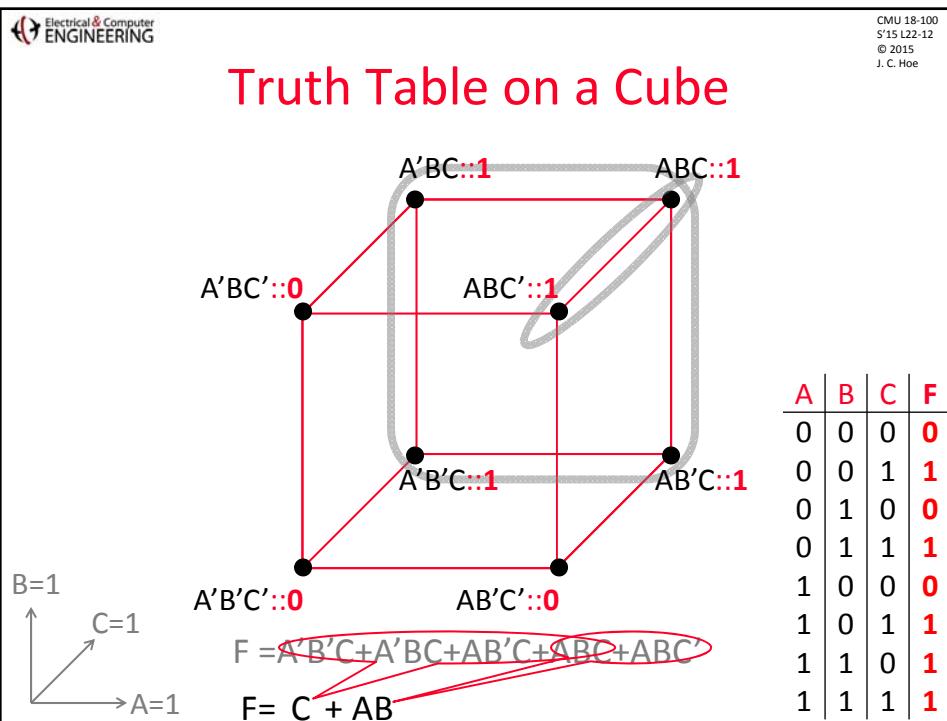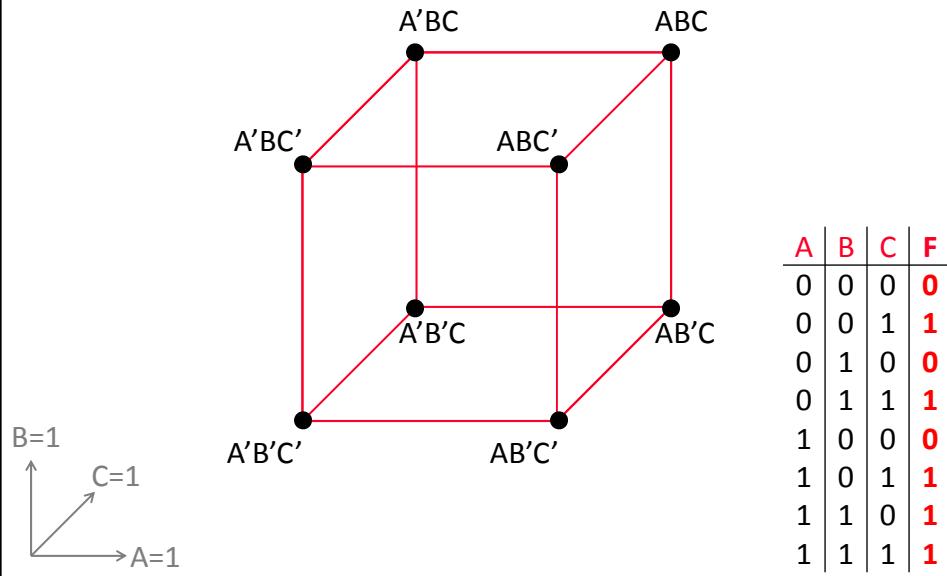


Karnaugh Map (K-map)

				<u>C=1 half</u>	
		A'=0	A'=1		
		A=0	A=1		
		A'B'C'	A'B'C	A'BC	A'BC'
	A=1 half	AB'C'	AB'C	ABC	ABC'

B=1 half

- ◆ Same as the 3-d cube before, but easier to draw

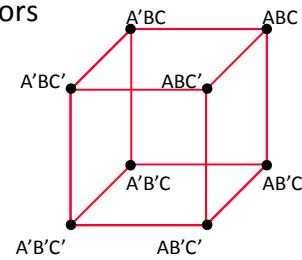- each minterm has 3 adjacent neighbors
- minterms that differ in only 1 input are adjacent
- any two adjacent minterms form a 1-d sub-cube
- any 4 minterms in a rectangle or square form a 2-d sub-cube



Karnaugh Map (K-map)

		<u>C</u>	
		A'=0	A'=1
		A=0	A=1
		0	1
	A=0	1	1
		1	0
		0	1

B

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


- ◆ $F = A'B'C + A'BC + AB'C + ABC + ABC'$
- ◆ $F = A'C + AC + AB = B'C + BC + AB$
- ◆ $F = C + AB$

each product is an "implicant" of F;
i.e., a sufficient condition for F


Finding minimum SOP corresponds to covering all members of the onset using the largest cubes possible without redundant cubes

4-Variable Hypercube (Example 12.11)

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

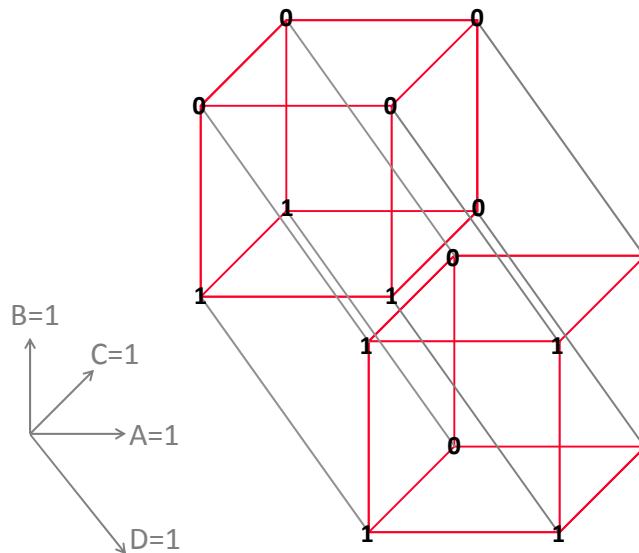

4-Variable K-map: Example 12.11

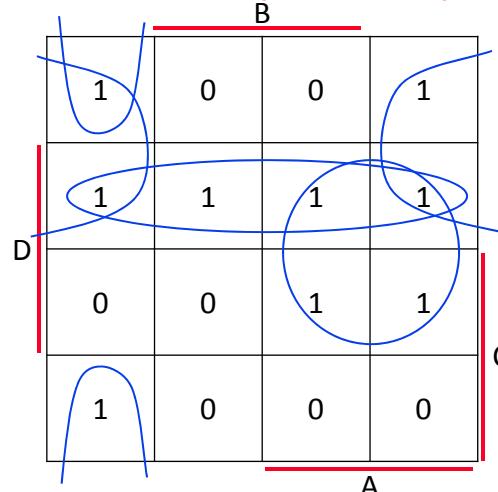

$$\begin{aligned}
 F = & AD + C'D \\
 & + B'C' \\
 & + A'B'D'
 \end{aligned}$$

Attempt to cover using, in order, 4-d, 3-d, 2-d, 1-d, 0-d (minterm) cubes

Stop when all members of the on-set are covered

Check for redundancies (Be sure to study examples in Rizzoni 12.4)

Does $XY + YZ + X'Z = XY + X'Z$?

	Z		
	0	1	1
X	0	0	1
Y			1

◆ Proof strategy I

- Expand XY , YZ , $X'Z$ to the 4 minterms
- Unite XYZ and XYZ' to XY ; unite $X'YZ$ and $X'Y'Z$ to $X'Z$

◆ Proof strategy II

- expand YZ to minterms XYZ and $X'YZ$
- XYZ absorbs into XY ; $X'YZ$ absorbs into $X'Z$

Does $XY + YZ + X'Z = XY + X'Z$?


$$\begin{aligned}
 & XY + YZ + X'Z \\
 &= XY \cdot 1 + YZ \cdot 1 + X'Z \cdot 1 && \text{rule 6} \\
 &= XY(Z+Z') + YZ(X+X') + X'Z(Y+Y') && \text{rule 4} \\
 &= XYZ + XYZ' + YZX + YZX' + X'ZY + X'ZY' && \text{rule 14} \\
 &= XYZ + XYZ' + XYZ + X'YZ + X'YZ + X'Y'Z && \text{rule 11} \\
 &= XYZ + XYZ' + XYZ' + X'YZ + X'YZ + X'Y'Z && \text{rule 10} \\
 &= XYZ + XYZ' + X'YZ + X'Y'Z && \text{rule 3} \\
 &= XY(Z+Z') + X'Z(Y+Y') && \text{rule 14} \\
 &= XY \cdot 1 + X'Z \cdot 1 && \text{rule 4} \\
 &= XY + X'Z && \text{rule 6}
 \end{aligned}$$

Does $XY+YZ+X'Z=XY+X'Z$? (done another way)


$$\begin{aligned}
 & XY+YZ+X'Z \\
 = & XY+YZ \cdot 1 + X'Z && \text{rule 6} \\
 = & XY+YZ(X+X') + X'Z && \text{rule 4} \\
 = & XY+YZX+YZX'+X'Z && \text{rule 14} \\
 = & XY+XYZ+X'ZY+X'Z && \text{rule 11} \\
 = & XY+XYZ+X'Z+X'ZY && \text{rule 10} \\
 = & XY \cdot 1 + XYZ + X'Z \cdot 1 + X'ZY && \text{rule 6} \\
 = & XY(1+Z) + X'Z(1+Y) && \text{rule 14} \\
 = & XY \cdot 1 + X'Z \cdot 1 && \text{rule 2} \\
 = & XY+X'Z && \text{rule 6}
 \end{aligned}$$

} rule 15
 absorption

Don't Care

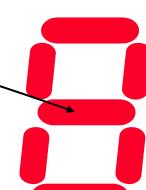- ◆ BCD code encodes a decimal digit using 4 bits
 - 0_{10} as 0000_2 ; 1_{10} as 0001_2 ;; 9_{10} as 1001_2
 - the patterns $1010_2 \sim 1111_2$ are not used
- ◆ Suppose F controls the on/off of this segment of a 7-segment display
 - $F = \begin{cases} 1 & \text{for } 0010, 0011, 0100, 0101, 0110, 1000, 1001 \\ 0 & \text{for } 0000, 0001, 0111 \\ \text{"don't care"} & \text{for } 1010 \sim 1111 \end{cases}$
- ◆ In a K-map, "don't care" can have cake and eat it too
 - treat them as 1s to enable larger cube covers
 - but also okay to leave uncovered (like 0s)


4-Variable Example with Don't Care

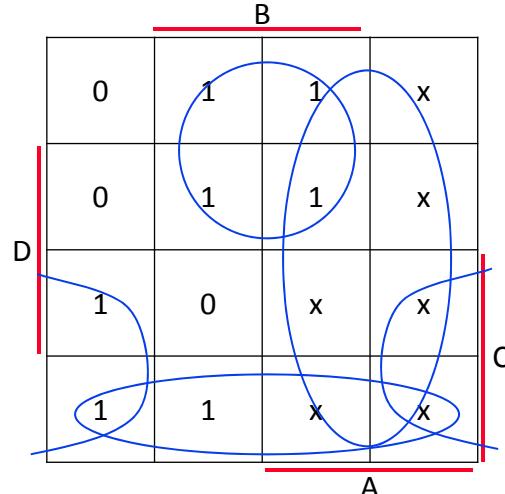

$$F = BC' + CD' + B'C$$

$$F = \begin{cases} 1 & \text{for } ABCD = 0010, 0011, 0100, 0101, 0110, 1000, 1001 \\ 0 & \text{for } ABCD = 0000, 0001, 0111 \\ \text{"don't care"} & \text{for } ABCD = 1010 \sim 1111? \end{cases}$$

Tricky K-map Example

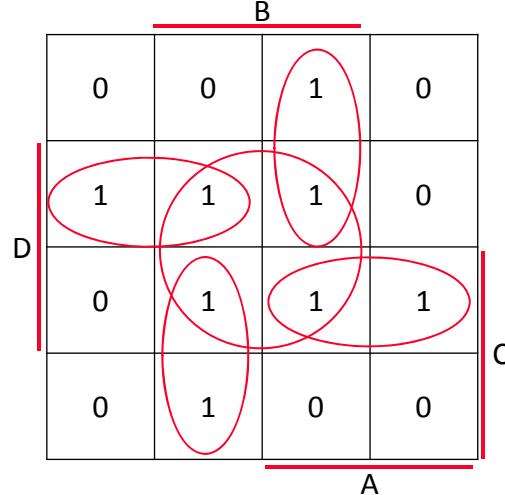

Following the simple K-map recipe will result in a redundant cover in this example.

Useful K-map Conventions

- ◆ Think of min-terms in a truth table like binary numbers
- ◆ With N inputs, count from 0 to 2^N-1
- ◆ For example, N=4

W	X	Y	Z	corresponding minterm
0	0	0	0	$W'X'Y'Z'$
0	0	0	1	$W'X'Y'Z$
0	0	1	0	$W'X'YZ'$
0	0	1	1	$W'X'YZ$
⋮	⋮	⋮	⋮	
1	1	0	1	$WXY'Z$
1	1	1	0	$WXYZ'$
1	1	1	1	$WXYZ$

Useful K-map Conventions

- ◆ Consistency saves time and reduces errors, e.g., N=4
 - vary the 2 more significant bits (WX) left-and-right
 - vary the 2 less significant bits (YZ) up-and-down.
- ◆ Transcribing from T-table to K-map by Gray counting
 - the neighboring columns (or rows) differ by only 1 bit
 - 00->01->11->10 (and not 00->01->10->11)

