

## 18-100 Lecture 24: Sequential Logic Design

James C. Hoe  
Dept of ECE, CMU  
April 21, 2015

Today's Goal: Start thinking about stateful stuff

Announcements: Read Rizzoni 12.6

HW 9 due

Exam 3 on April 30

Final Exam, Fri., May 8, 8:30~11:30, GHC 4401 *Conflicts?*


Handouts: HW 10 (on Blackboard)

HW 9 solutions (on Blackboard later on)

Lab 12 (on Blackboard later on)
 
## Let's refresh our memory....


- ◆ All “sequential” digital systems comprise



- input and output
- state stuff that remembers
- “combinational” stuff that computes a function (has no memory)
- ◆ In an execution, state is updated to a “next state” based on a function of the current state
 
## Memory 101


- ◆ Pure combinational logic always go from a **current** input to a **current** output without any looping back  
There is no notion of time, past or future
- ◆ To remember, must somehow incorporate **previous** values
- ◆ You mean like this?



Does it remember? What does it remember?  
(It is easier to see if you associate a small propagation delay with wires and gates)
 
## A Better Try: the SR Latch



- ◆ Keep in mind that
  - $X+0=X \Rightarrow (X+0)'=X'$
  - $X+1=1 \Rightarrow (X+1)'=0$
- ◆ Hint: **S** stands for “set”; **R** for “reset”
- ◆ Consider
  - **S=0** and **R=0**: the NORs simply act like inverters in the feedback loop; **Q** is remembered
  - **S=1** and **R=0**: the top NOR’s output is forced to 0; the bottom NOR inverts the feedback; **Q** is set to 1
  - **S=0** and **R=1**: the bottom NOR’s output is forced to 0; the top NOR inverts the feedback; **Q** is reset to 0
  - **S=1** and **R=1**: **Just don’t do it**  
After asserting **S** or **R**, the resulting **Q** is remembered when **S** and **R** are both deasserted again



If you feel brave try finding the “dual”

 
 
## Level-Sensitive D Latch

- ◆ E is “latch enable”
  - when E is asserted Q follows D combinationaly
  - when E is de-asserted the last Q value is remembered
- ◆ Timing Diagram



  
## Edge-Triggered D Flip-Flop

- ◆ Q follows D only at the “instant” of rising edge of clock
- ◆ Q independent of D at all other time
- ◆ Timing Diagram




Q only make  
“synchronous”  
transitions

# Synchronous Finite State Machines

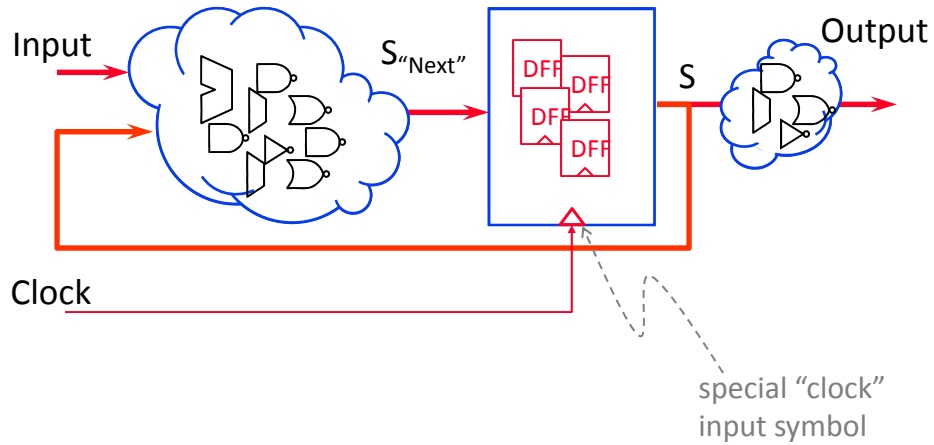

# Synchronous Timing (Simplified)


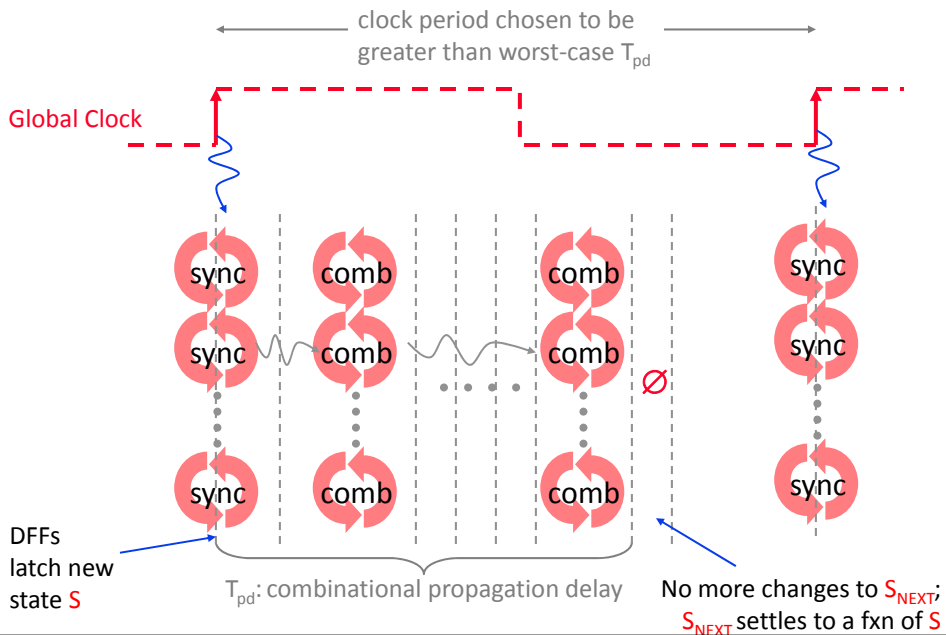


Let's play with this a bit first

## 1-bit FSM Example

- ◆ Implied input: **Reset**, **Clk**
- ◆ Input
  - 1-bit signal "**Tick**"
  - you can vary its value over time, anytime you like, but only the values at the rising clock edges matter
- ◆ Output
  - 1-bit signal "**Tock**"
  - **Tock** should be 0 after reset
  - **Tock** should become 1 and stay 1 after **Tick** has been 1 (as sampled on a rising clock edge)
- ◆ What are the two states?
  - **Tick** has never been 1 since reset
  - not the above


# 1-bit FSM Example

 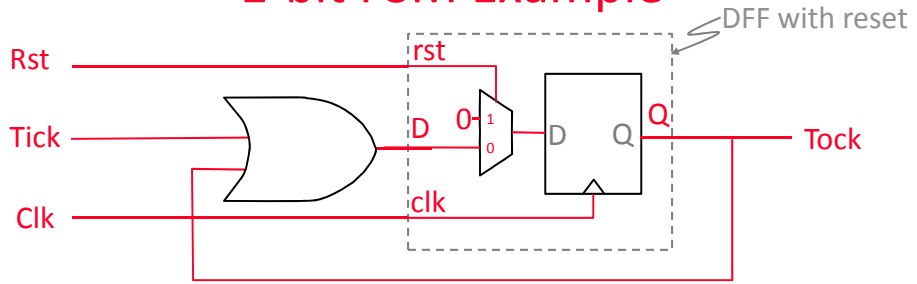

# FSM as an Abstraction

 
## State Transition Diagram

- ◆ A convenient FSM abstraction
- ◆ States (bubbles)
  - best to give each state a meaningful "name"
  - output value associated with each state (Moore machines)
  - one state is designated as the initialization state
- ◆ Transitions (edges)
  - edges are predicated by input conditions (i.e., follow this edge if condition is met)
  - each state must have transitions for all possible input values


 
## Let's play a bit more


- ◆ New design: **Tock** should become 1 and stay 1 after **Tick** has been 1 three consecutive times!



What if I want **Tock=1** only right after each time **Tick** has been 1 three consecutive times; **Tock=0** at all other times
 
## Realizing an FSM

- ◆ State assignment
  - require at least  $n = \lceil \lg_2 N \rceil$  bits  $Q_{n-1}, \dots, Q_0$  to encode an FSM with  $N$  states (each bit is a D flip-flop)
  - assign each state to a unique encoding
  - choice of encoding can affect the size of combinational next-state logic (don't worry about it in 18-100)
- ◆ Next-state logic
  - computes the next state value  $D_{n-1}, \dots, D_0$  as a function of the FSM input and current state  $Q_{n-1}, \dots, Q_0$
- ◆ "Moore-style" Output logic
  - computes the FSM output as a function of current state  $Q_{n-1}, \dots, Q_0$



## Tick-Tock Example


- ◆ 2 states, hence a 1-bit FSM
  - "no 1's" when  $Q_0=0$
  - "seen 1's" when  $Q_0=1$

- ◆ Next-state logic truth table

$Q_0$	Tick	$D_0$
0	0	0
0	1	1
1	0	1
1	1	1

- ◆ Output logic truth table


$Q_0$	Tock
0	0
1	1

 



# Three 1's Example


state assignment			next-state logic				output logic			
State	$Q_1$	$Q_0$	$Q_1$	$Q_0$	Tick	$D_1$	$D_0$	$Q_1$	$Q_0$	Tock
no info	0	0	0	0	0	0	0	0	0	0
saw 1	0	1	0	1	0	0	0	0	1	0
saw11	1	0	1	0	0	0	0	1	0	0
saw111	1	1	1	1	0	1	1	1	1	1
			1	1	1	1	1			

 

# Three 1's Example


$D_0$	Tick			
	0	1	0	0
$Q_1$	0	1	1	1
				$Q_0$

$D_1$	Tick			
	0	0	1	0
$Q_1$	0	1	1	1
				$Q_0$

 

 
## Why FSMs?

- ◆ Looking for 0s and 1s . . . . . (this is actually serious computer science; look up “regular expressions” on Wikipedia)
- ◆ Simple computation/calculations




- ◆ The first and foremost practical use is to sequence the control of a “datapath” or a “system”

## Atmel ATmega8 Datapath

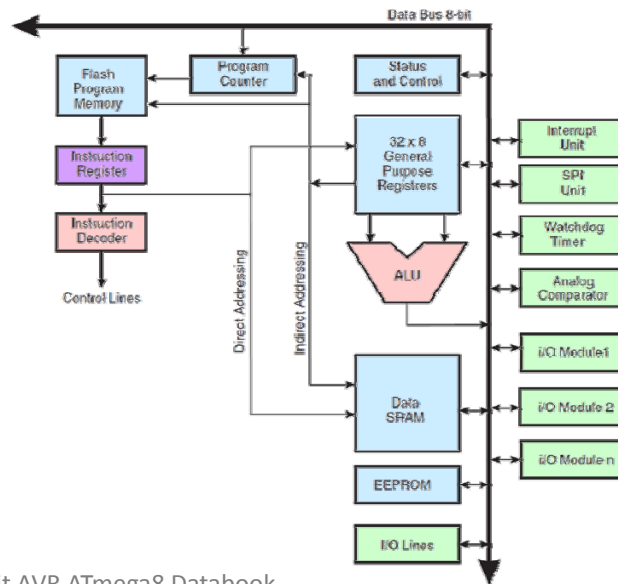
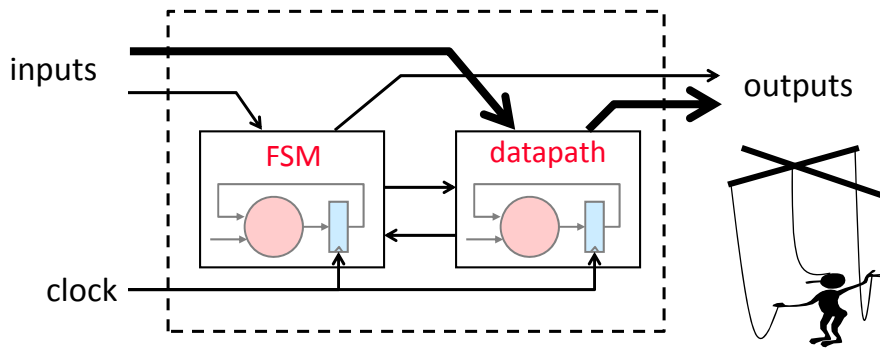
## FSM-D

- ◆ datapath = combinational logic and registers to carry out computation (puppet)
- ◆ FSM = combinational logic and registers for control and sequencing (puppeteer)



## SR Latch "Dual"

