

18-100 Lecture 23: Combinational Datapath

James C. Hoe
Dept of ECE, CMU
April 14, 2015

Today's Goal: Structured combinational digital circuits
Announcements: Read Rizzoni 12.4 and 12.5
 Read Rizzoni 12.6 for next time
 Exam 3 on April 30
 Final Exam, Fri., May 8, 8:30~11:30, GHC 4401 *Conflicts?*
 HW9 due Tuesday 4/21
 No class on Thursday; no lab this week


Handouts:

Combinational Logic Blocks


- ◆ With K-map, you can build any combinational functions you want, but not everything should be build from K-map
 - minimum SOP/POS \neq globally "optimum"
 - some functions have special structures to be taken advantage of
 - some functions are so frequently used they have become conventions
- ◆ Major examples
 - multiplexer
 - demultiplexer
 - encoder/decoder of various types
 - arithmetic: adder, multiplier, etc
 - read-only memory

Multiplexer (aka mux)

 - Simplest form is a 1-bit 2-to-1 multiplexer



 - This is the hardware “if-then-else”;
O gets either D_0 or D_1 depending on S




S	D_0	D_1	O
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

or simply


S	O
0	D_0
1	D_1

4-to-1 Mux Example

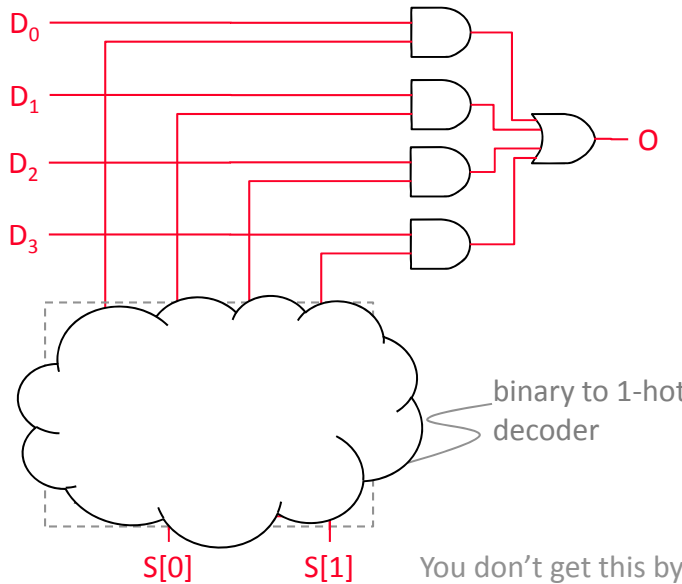


Multiplexer Generalizations

 - ◆ N-to-1 selection using
 - S of $\lg_2 N$ bits as a binary number
 - or
 - S of N bits as a "one-hot" bit mask (this is called a decoded mux)




 - ◆ D_x and O could be a bundle of wires of width w (aka a bus), e.g., to carry a binary number



Demultiplexer (aka demux)

- ◆ Example: 1-bit 1-to-2 demultiplexer

 


S	D	O ₀	O ₁
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1

or simply


S	O ₀	O ₁
0	D	0
1	0	D

 - ◆ Generalizable to 1-to-N demux'ing
- ◆ Does it also make sense to demux a bus?



if $D=1$, O is 1-hot of S


1-to-4 Demux Example

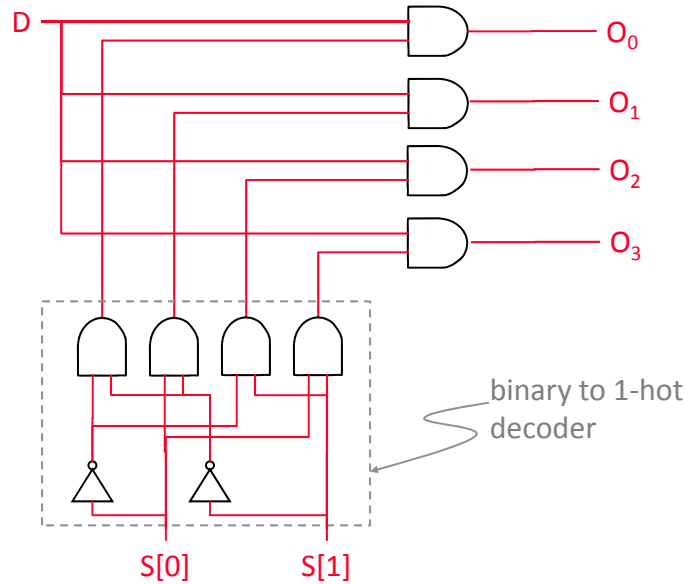

Encoders/Decoders


- ◆ Mapping between well-known representations, e.g.,
 - between binary and 1-hot
 - between BCD and binary
 - from BCD to 7-segment display
- ◆ Mapping input to well-known output functions
 - e.g., priority encoder
 - input: 1-bit inputs from N requesters
 - output: $n = \lceil \lg_2 N \rceil$ bit binary value that chooses the lowest number'ed requester asserting R

What is S if no one is requesting?

 


(Unsigned) Binary Addition

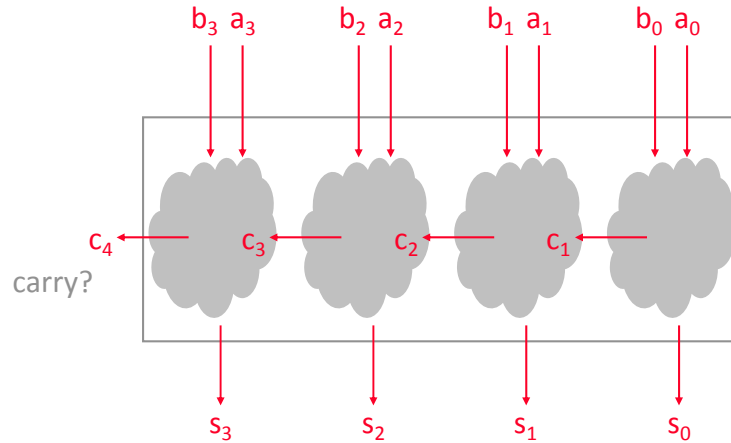- How to add **A** and **B**, each 4 bits, by long hand



Full Adder

 

c_{in}	a	b	c_{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = bc_{in} + ac_{in} + ab$$


3-way majority parity

a, b, c_{in} are functionally indistinguishable as inputs

Unsigned Binary Addition

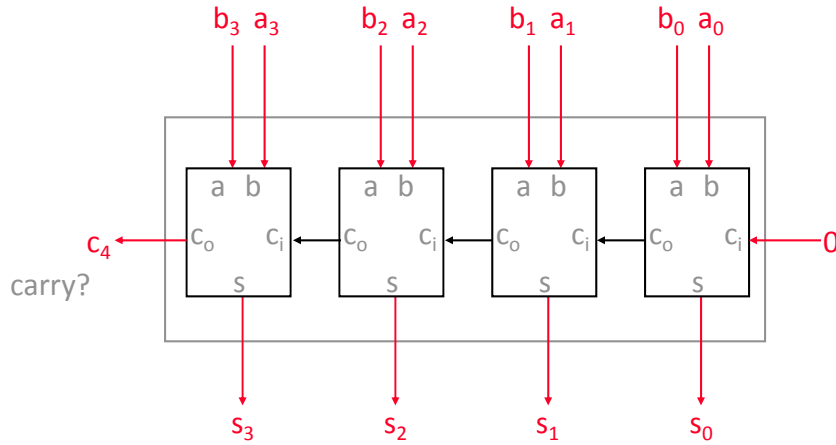


2's-Complement Addition

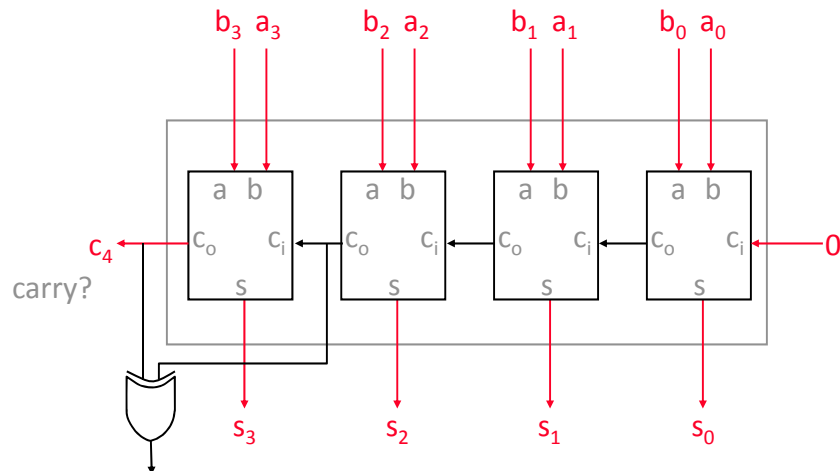

overflow? = if $(a_3 \oplus b_3)$ then false else $(a_3 \oplus s_3)$
 - can't overflow when adding a pos. and a neg. number
 - if 2 pos. numbers yield a neg. number $\Rightarrow V$; vice versa

2's-Complement Subtraction

 
- ◆ Subtracting is like adding the negative
- ◆ Negation is easy in a 2's-complement representation



How do you build a comparator (i.e., $>$, $<$)?

Cost and Speed of an n-bit "Ripple-Carry" Adder

 
- ◆ Cost is $n \times \text{SizeOf}(\text{ Full Addder })$
- ◆ S and C_{out} do not change instantaneously when a and b are changed
 - longest delay (aka Critical Path Delay) is from a_0, b_0 , or C_{in} to S_{n-1} or C_{out}
 - $n \times \text{DelayOf}(\text{ Full Addder })$
 - $n \times 2$ gate delays (assuming 2-level SOP is used)



BTW, ripple-carry is adder design for babies


Prefix Carry-Look-Ahead

Example: 8-bit, 2-ary CLA

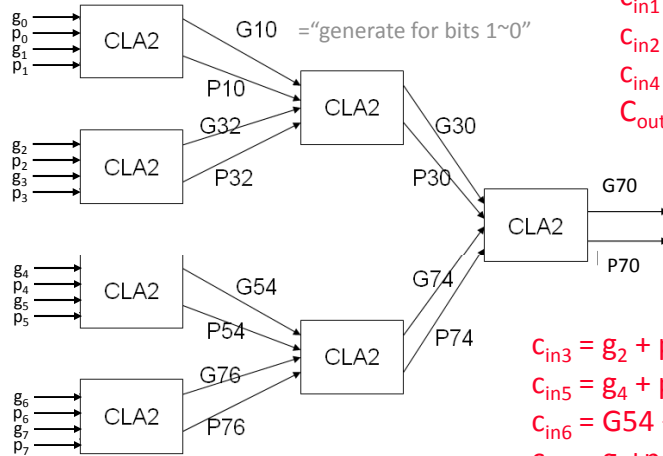

Read-Only Memory (ROM)

 
- ◆ Input: an n -bit address
- ◆ Output: data of width w stored at location $ROM[addr]$ (2^n such locations)



- ◆ Since it is read-only, the ROM's contents have to be initialized by an offline process
- ◆ Since it is read-only, a ROM is combinational!!
 - the same **addr** always returns the same answer
 - an ROM is an n -input combinational function; each address is a minterm; reading $ROM[addr]$ is like reading the truth table
 - it is actually a reasonable way to implement some very irregular combinational functions

Let's refresh our memory....

 
- ◆ All “sequential” digital systems comprise



- input and output
- state stuff that remembers
- “combinational” stuff that computes a function (has no memory)
- ◆ In an execution, state is updated to a “next state” based on a function of the current state

Memory 101

 - ◆ Pure combinational logic always go from a **current** input to a **current** output without any looping back
There is no notion of time, past or future
- ◆ To remember, must somehow incorporate **previous** values
- ◆ You mean like this?



Does it remember? What does it remember?
(It is easier to see if you associate a small propagation delay with wires and gates)