

## 18-100 Lecture 25: More Finite State Machines

James C. Hoe  
Dept of ECE, CMU  
April 23, 2015

Today's Goal: Let's make it a wrap!


Announcements: Exam 3 on April 30  
Final Exam, Fri., May 8, 8:30~11:30, GHC 4401  
HW 10 due on Tuesday

Handouts:

## Another Example: Up-down Counter


- ◆ Input: 1-bit (**U**)p  
1-bit (**D**)own
- ◆ Output: 2-bit unsigned binary value: 0, 1, 2, or 3
- ◆ What to do:
  - output should initialized to 0
  - if **U** and **D** are both deasserted, output should stay at the same value (after the next clock edge)
  - if **U** and **D** are both asserted, output should reset to 0
  - if only **U** is asserted, output should count up; if output is already 3, output stays at 3
  - if only **D** is asserted, output should count down; if output is already 0, output stays at 0

# Up-down Counter

 

UD  
00=keep  
01=count dwn  
10=count up  
11=reset

# Up-down Counter

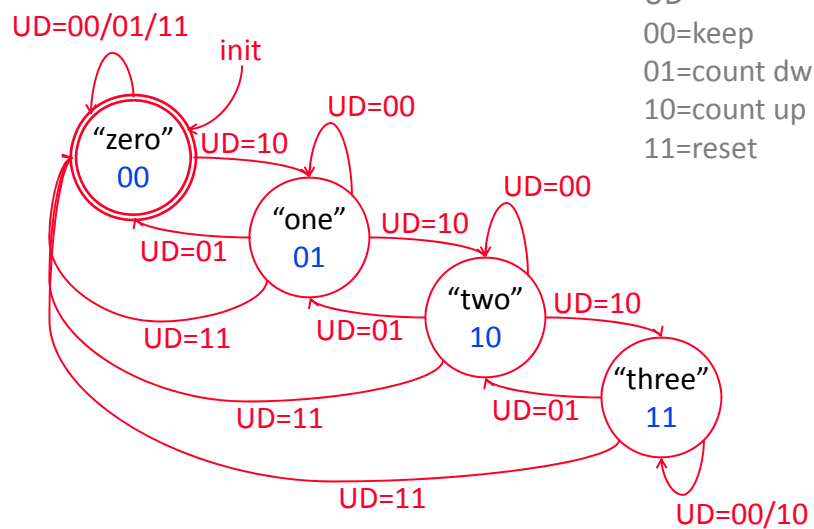


UD  
00=keep  
01=count dwn  
10=count up  
11=reset

What state encoding would you choose?

## My All-Time Favorite FSM


- ◆ Input: 1-bit **I**
- ◆ Output: 1-bit **O**
- ◆ What to do:
  - output **O** should be 1 each time after observing the sequence 1011 on input **I**
  - output **O** should be 0 at all other times
  - e.g.,
    - I: 101011010010110111111 ...
    - O: 000000**1**0000000**1**00**1**000 ...

## Looking for 1011

 

Picking good state names is very important

## Looking for 1011

 

Picking good state names is very important

## Next-State and Output Logic


State	$Q_2$	$Q_1$	$Q_0$	I	$D_2$	$D_1$	$D_0$
"??"	0	0	0	0	_____	_____	_____
				1	_____	_____	_____
"1"	0	0	1	0	_____	_____	_____
				1	_____	_____	_____
"10"	0	1	0	0	_____	_____	_____
				1	_____	_____	_____
"101"	0	1	1	0	_____	_____	_____
				1	_____	_____	_____
"1011"	1	0	0	0	_____	_____	_____
				1	_____	_____	_____

State	$Q_2$	$Q_1$	$Q_0$	O
"??"	0	0	0	_____
"1"	0	0	1	_____
"10"	0	1	0	_____
"101"	0	1	1	_____
"1011"	1	0	0	_____


## Next-State and Output Logic

State	$Q_2$	$Q_1$	$Q_0$	$I$	$D_2$	$D_1$	$D_0$	Next State	Output $O$
"??"	0	0	0	0	0	0	0	"??"	0
				1	0	0	1	"1"	0
"1"	0	0	1	0	0	1	0	"10"	0
				1	0	0	1	"1"	0
"10"	0	1	0	0	0	0	0	"??"	0
				1	0	1	1	"101"	0
"101"	0	1	1	0	0	1	0	"10"	0
				1	1	0	0	"1011"	0
"1011"	1	0	0	0	0	1	0	"10"	0
				1	0	0	1	"1"	1
	1	0	1	*	*	*	*	*	*
	1	1	0	*	*	*	*	*	*
	1	1	1	*	*	*	*	*	*

## Mealy vs. Moore

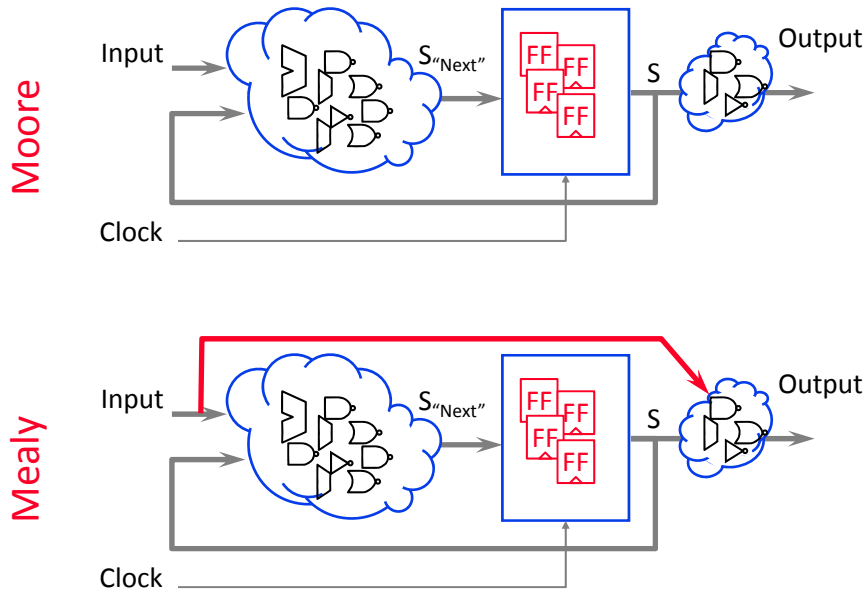


## Looking for 1011 (Mealy)

 

The output in a given state also depends on current input

## Looking for 1011 (Mealy)

 

The output in a given state also depends on current input

## Mealy FSM Logic

next-state logic

State	$Q_1$	$Q_0$	$I$	$D_1$	$D_0$
“??”	0	0	0	0	0
			1	0	1
“1”	0	1	0	1	0
			1	0	1
“10”	1	0	0	0	0
			1	1	1
“101”	1	1	0	1	0
			1	0	1


output logic

State	$Q_1$	$Q_0$	$I$	$O$
“??”	0	0	0	0
			1	0
“1”	0	1	0	0
			1	0
“10”	1	0	0	0
			1	0
“101”	1	1	0	0
			1	1

We are done! Time for some fun!
 
# FSM-D

- ◆ datapath = combinational logic and registers to carry out computation (puppet)
- ◆ FSM = combinational logic and registers for control and sequencing (puppeteer)




# Multiply 2 n-bit numbers: $a \times b$


- ◆ Given unsigned numbers  $a_{n-1}a_{n-2}\dots a_2a_1a_0$  and  $b_{n-1}b_{n-2}\dots b_2b_1b_0$

$$a \cdot b = \sum_{j=0}^{n-1} \left( 2^j b_j \left( \sum_{i=0}^{n-1} 2^i a_i \right) \right)$$

 - ◆ Construct a full adder array where the summand ( $a_{n-1:0} \times 2^i$ ) can be conditionally zero'ed according to  $b_i$  of  $b_{n-1:0}$



 
- ◆ 2n bits are required to represent all possible products without overflow



2's complement?




# Iterative Shift-and-Add Multiplication

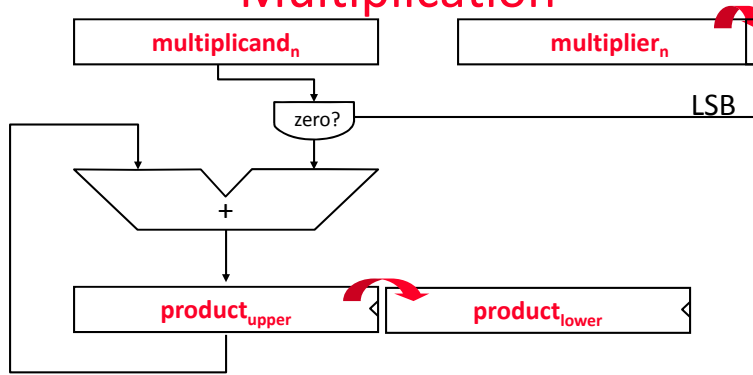


- ◆ To start, set multiplier/multiplicand and zero product
- ◆ Require  $n$  iterations of “shift-and-add”
  - add either 0 or multiplicand depending on LSB of multiplier
  - shift both multiplier and product


# DFF Varieties

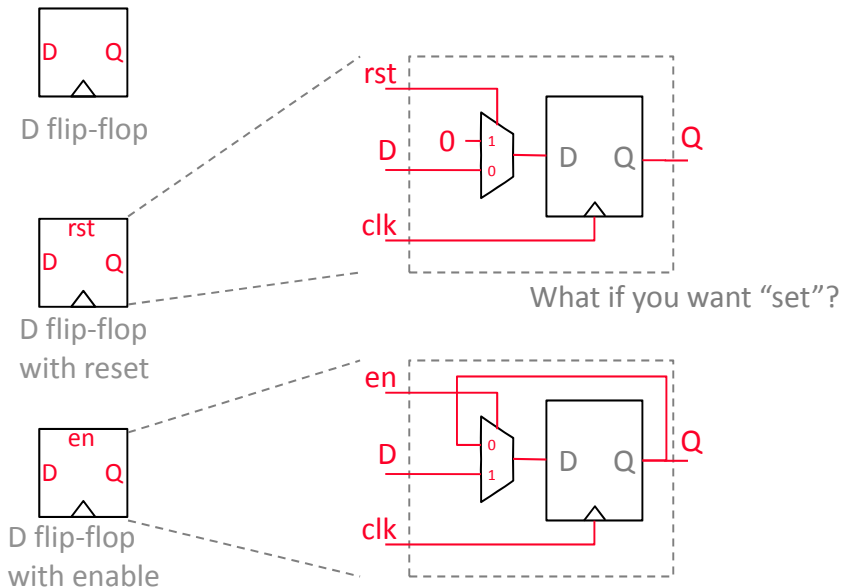

## Register (DFFs with common control)

 


## Shift Register

 

Set mux to **(e)**nable to latch new value  
**(s)**hift to shift current value by 1 position  
**(k)**eep to remember the current value
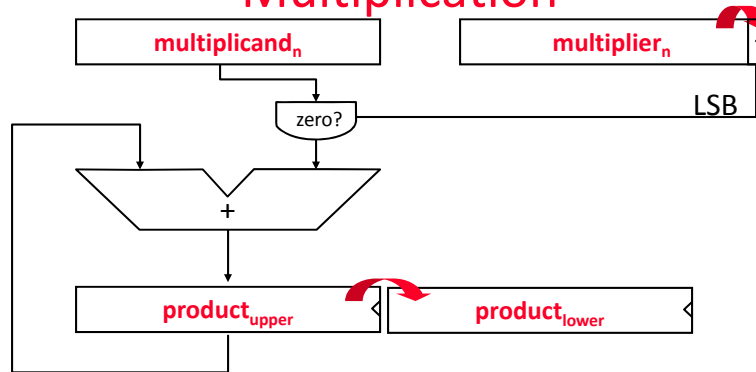
## Iterative Shift-and-Add Multiplication




- ◆ To start, set multiplier/multiplicand and zero product
- ◆ Require  $n$  iterations of “shift-and-add”
  - add either 0 or multiplicand depending on LSB of multiplier
  - shift both multiplier and product


## FSM Controller

- ◆ User input: 1-bit (**G**)o
- ◆ User output: 1-bit (**R**)eady
- ◆ Control output (to datapath):
  - 1-bit (**N**)ew: - latch new multiplier and multiplicand  
- zero the product register
  - 1-bit (**S**)hift: - shift the multiplier register  
- latch-and-shift the product register
- ◆ What to do
  - the user can assert **G** (for 1 clock edge) whenever **R** is asserted to begin a new multiplication
  - controller asserts **N** to latch new multiplicand and multiplier; **R** should be de-asserted until finished
  - controller should assert **S** for  $n$  cycles, after which
  - controller should assert **R**, de-assert **S** and wait for the next **G** trigger to start over

## State Transition Diagram (say $n=4$ )

 




## State Transition Diagram (say $n=4$ )

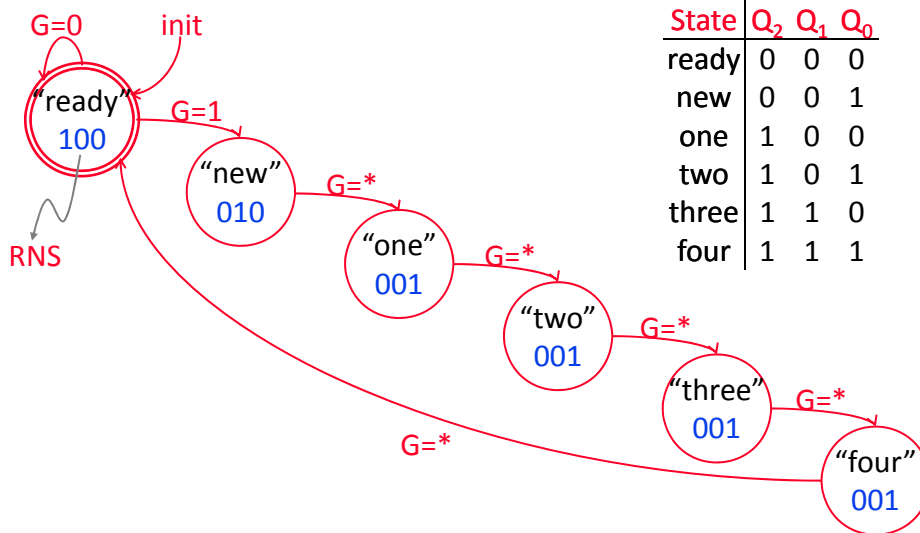

## Next-State Logic

next-state logic

$Q_2$	$Q_1$	$Q_0$	$G$	$D_2$	$D_1$	$D_0$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

 
 
 


$D_0 =$   
 $D_1 =$   
 $D_2 =$

## Next-State Logic

next-state logic

$Q_2$	$Q_1$	$Q_0$	$G$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	x	x	x
0	1	0	1	x	x	x
0	1	1	0	x	x	x
0	1	1	1	x	x	x
1	0	0	0	1	0	1
1	0	0	1	1	0	1
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	0	0	0
1	1	1	1	0	0	0

   

$D_0 = Q_2 Q_0' + Q_0' G$   
 $D_1 = Q_1 Q_0' + Q_2 Q_1' Q_0$   
 $D_2 = Q_2 Q_0' + Q_2 Q_1' + Q_1' Q_0$

The choice of state encoding helped here

## Output Logic

State	$Q_2$	$Q_1$	$Q_0$	R	N	S
ready	0	0	0	1	0	0
new	0	0	1	0	1	0
unused	0	1	0	x	x	x
unused	0	1	1	x	x	x
one	1	0	0	0	0	1
two	1	0	1	0	0	1
three	1	1	0	0	0	1
four	1	1	1	0	0	1

$$R = Q_2' Q_0'$$

$$N = Q_2' Q_0$$

$$S = Q_2$$

The choice of state encoding  
made a **REALLY BIG**  
difference here


(Try repeating this example  
with a random state  
assignment on your own)

## What we didn't talk about

- ◆ Cooperating Finite State Machines (CFSM)
  - many real designs have too many state bits to be designed as FSMs directly (e.g., a microprocessor)
  - must decompose by functionality and structure into manageable chunks (we saw FSM-D decomposition)
- ◆ Other timing disciplines, e.g.,
  - latch-based designs
  - dynamic logic
  - "asynchronous" logic
- ◆ Array memory structures and technologies
- ◆ Programmable logic devices

**18-240 is waiting for you**

## Computer System Abstraction Layers

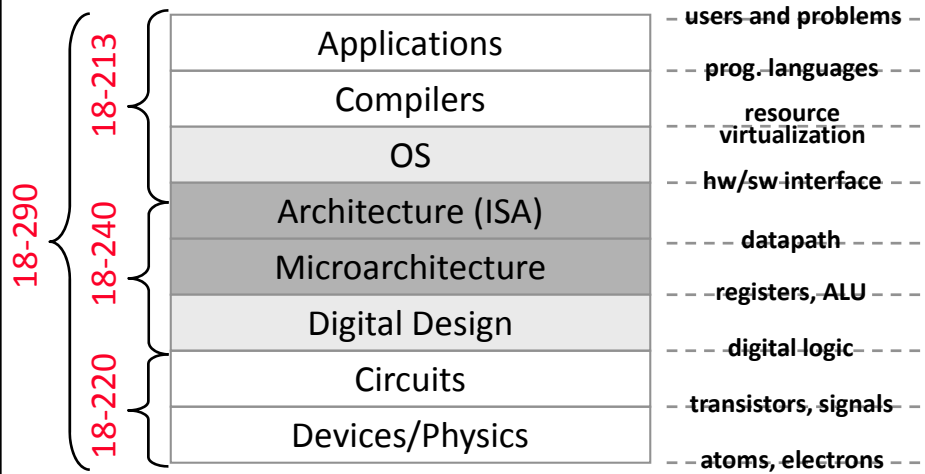

To use an abstraction properly you must understand the limits of the abstraction