18-643 Lecture 2: Basic FPGA Fabric

James C. Hoe

Department of ECE

Carnegie Mellon University


Housekeeping

- Your goal today: know enough to build a basic FPGA (even if not a very good one)
- Notices
 - Complete survey on Canvas, due noon, 9/6
 - Handout #2: lab 0, due noon, 9/11
 - Make friends, make teams, due noon, 9/11
- Readings (see lecture schedule online)
 - Altera 2006 white paper (see lecture schedule)
 - skim databooks referenced for more details

What it means:


"Field Programmable" "Gate Array"

SSI MSI LSI VLSI

 

From Quora, "How did people design integrated circuits in early years?"

How to democratize 100K gates

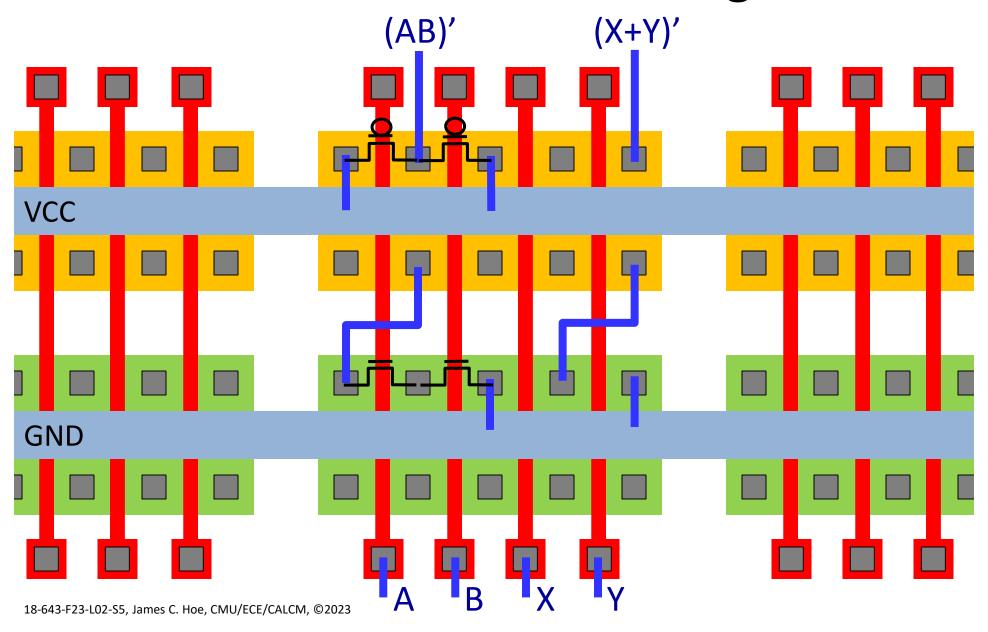

Idea behind Gate Arrays

- Mass produce identical gate array wafers
- Finish into <u>any design</u> by custom metal layers (2)
 - so called Mask-Programmable GA (MPGA)
 - reduced design effort (more automation, no layout)
 - reduced mask and fab cost
 - faster fab turn-around
- Proliferation of ASIC design starts
 - don't need volume for economy of scale
 - small design team could keep up with Moore's law

Of course, not as efficient as full-custom or standard-cell designs




How about no mask, no fab? i.e., "field programmable"


- Again, mass produce identical devices but this time fully-finalized
- Then what can still be changed after fab?

connections

– SRAM EPROM

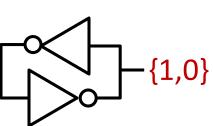

{1,0}

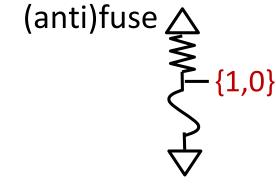

pass gate

mux

diode





Configurable "Logic Gates"




Reconfigurable Logic

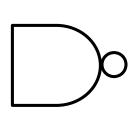 Arbitrary logic (combinational and sequential) can be formed by wiring up enough NANDs or muxes



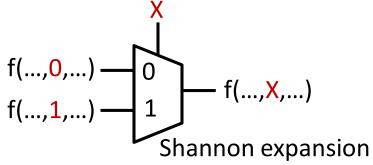

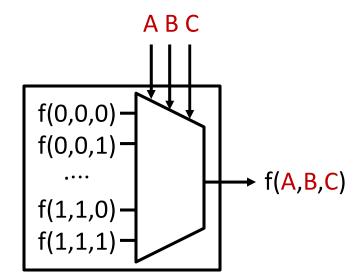- Lookup table as universal logic primitive
 - arbitrary n-input function
 from 2ⁿ-entry table
 - this is 8-by-1 bit "memory"



Size of Lookup Tables (aka LUTs)

- n-input function from 2ⁿ-entry LUT
- Count only the 6T SRAM cells, an n-LUT has 6·2ⁿ T
- Some points of reference
 - 2-input NAND = 4T
 - 3-input NAND = 6T
 - 3-input full-adder (a, b, c_{in})

•
$$s = a \oplus b \oplus c_{in} = 8T$$

•
$$c_{out} = bc_{in} + ac_{in} + ab = 18T$$

- 10-input 5-bit adder = 130T
- basic flip-flop=16T

muxes? (compare to 2 LUTs per latch)

24
48
96
192
384
768
1536
3072
6144

Choosing LUT Granularity

- Small LUTs
 - + shorter propagation delay (per LUT)
 - a given fxn consumes many LUTs (comes with wiring cost and delay)
 this kind
 - high "interpretation overhead" if too small
- Big LUTs
 - longer propagation delay (per LUT)
 - + a given fxn consumes fewer (but bigger) LUTs
 - high "interpretation overhead" if too large (and fxn has exploitable structure, e.g., 5-bit ripple add)
 - wastage if not all input are used in a LUT

Where is the sweetspot?

A Quantitative Look at LUT Sizing e.g., 2006 Altera White Paper on Stratix-II ALMs

Figure 4. Delay-Cost Tradeoff with LUT Size


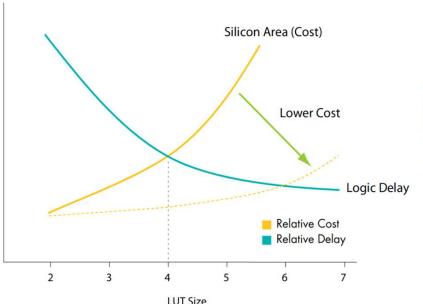


Figure 5. Distribution of Functions Generated by Synthesis

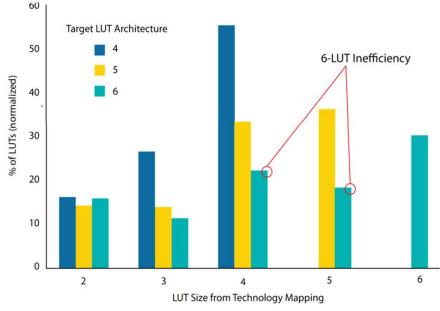


Large-enough functions have shorter total delay using bigger LUTs

But, bigger LUTs cost more and prone to "internal fragmentation"

4-LUTs 50+% fully utilized 6-LUTs less than 40% fully utilized


No one LUT size optimal ⇒ "adaptive" LUT approach

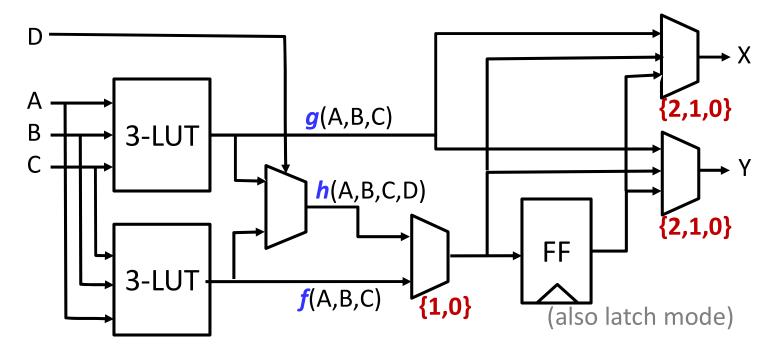LUT-based Configurable Logic Block (simplified sketch)



- 2 fxns (f & g) of 3 inputs OR 1 fxn (h) of 4 inputs
- hardwired FFs (too expensive/slow to fake)
- Just 10s of these in the earliest FPGAs

Xilinx XC2000 CLB (1980s)

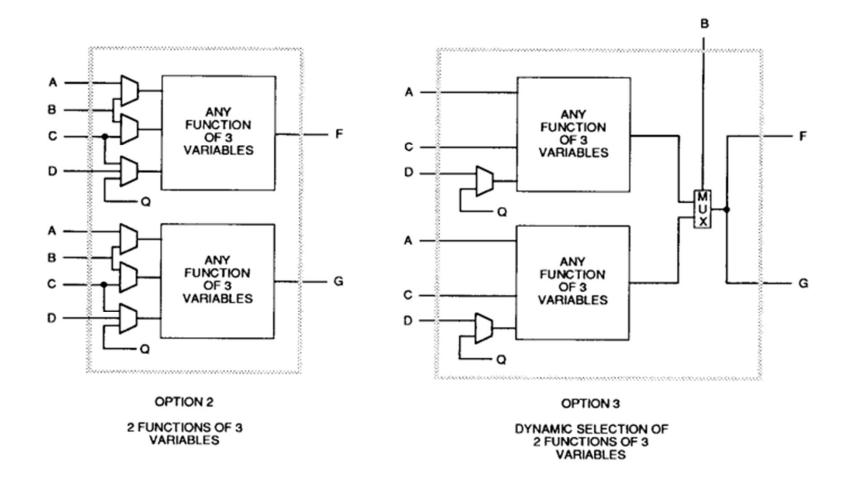

[XC2064, XC2018 Logic Cell Array]

Contemporary Xilinx CLB Architecture

 each 6LUT is two 5LUTs

 LUTs can also be used as small SRAMs

 special paths for addition and multiplexer

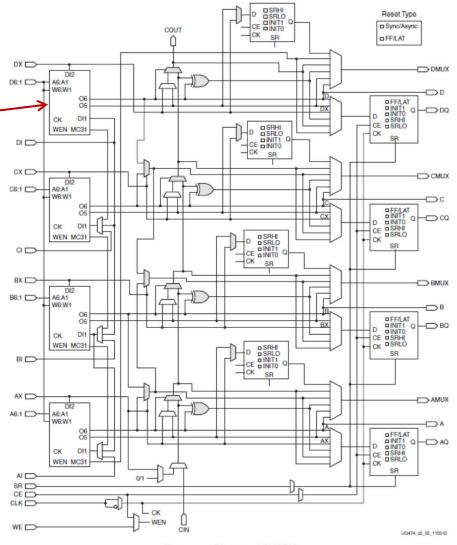


Figure 2-3: Diagram of SLICEM

2 slices per CLB

Largest devices (many \$K each) have several 100K slices

in 2022 has over 1M slices

[Figure 2-3: 7 Series FPGAs CLB User Guide]

Still Coarser Logic Blocks?

- So called Coarse-Grain Reconfigurable Arrays (CGRAs) based on complete adders or ALUs
 - native arithmetic units have low interpretation overhead if you are doing arithmetic
 - poor fit if you are working with narrow data or bitlevel manipulations
- Even coarser is to use many tiny processors
 - still a spatial computing paradigm
 - not programmed with RTLs
 - converging with software multicores

Brief Aside: Mapping Logic To LUTs

- Start from primary output and input to registers,
 cover logic graph with cuts of less than K input edges
- K-cuts corresponding to K-LUT realizable functions

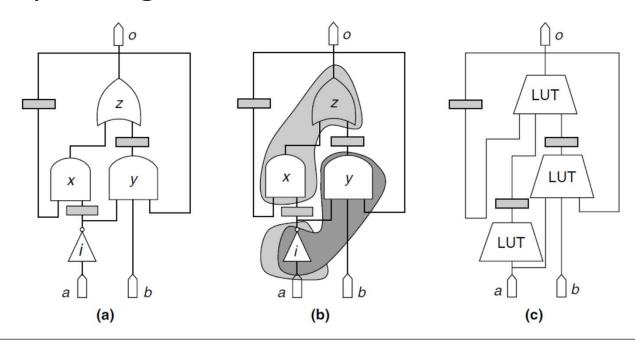



FIGURE 13.1 ■ Structural technology mapping: (a) original network, (b) covering, and (c) mapping solution.

[Figure 13.1: "Reconfigurable Computing: The Theory and Practice of FPGA-Based Computation"]

Placement




... and Route

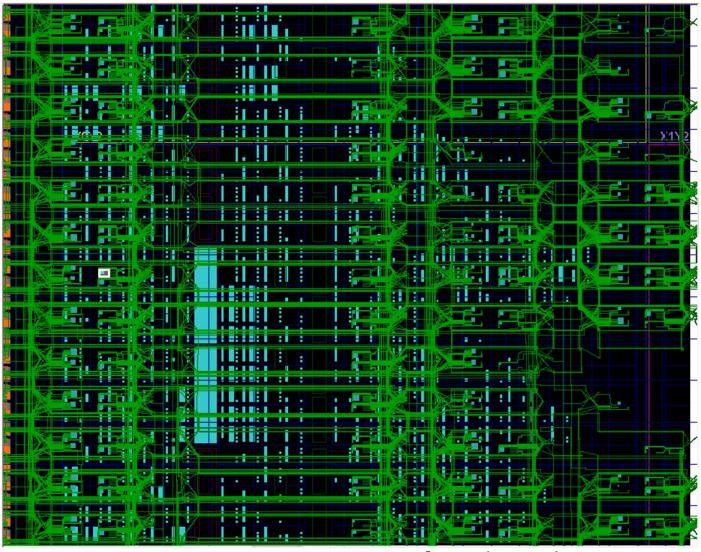


Configurable "Wires"

PLA-style Configurable Routing

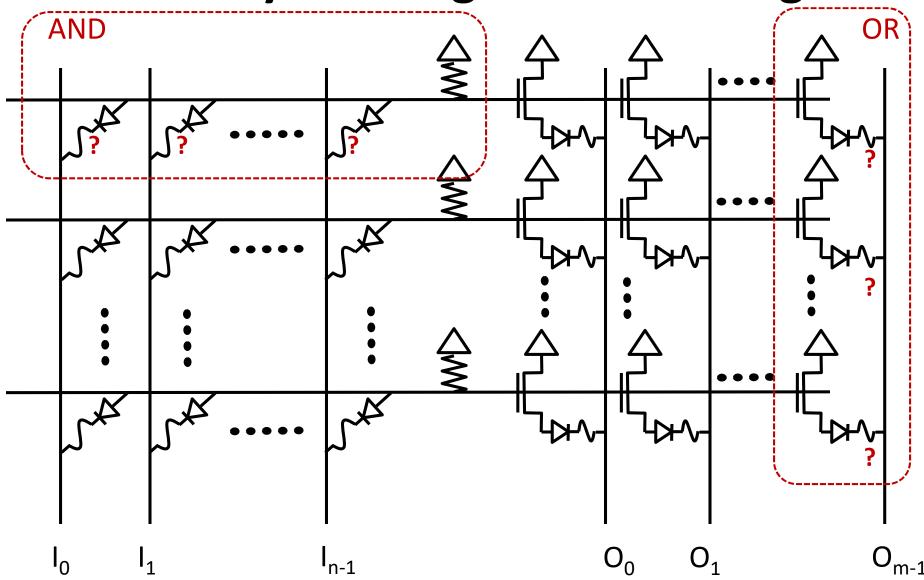


Island Style Routing Architecture

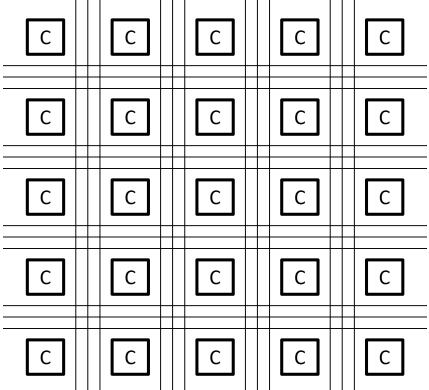- CLB islands in sea of interconnects
- Flexible routing to support ASIC style netlists
- Note regularity in structure





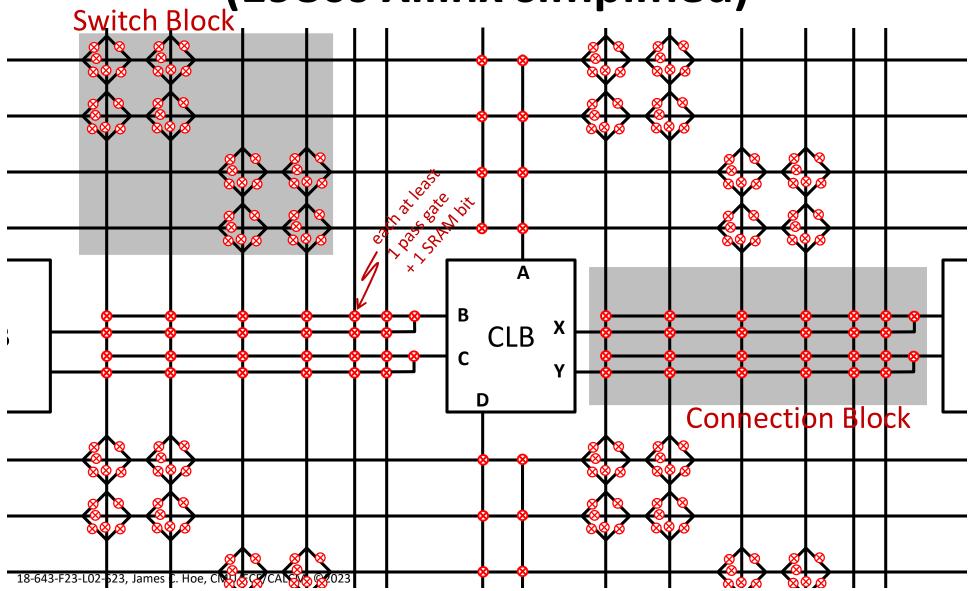Configurable Routing (1980s Xilinx simplified)



Reconfigurable Routing is Expensive!

- Routing resource area is on par with logic
- Each configurable connection is
 - area of configuration bit
 - area of configurable connection

and don't forget propagation delay

- Too much: cost for everyone who doesn't need it
- Too little: congestion leaves unreachable CLBs unused
 - worse for larger arrays/designs (why?)
 - buy a \$10K FPGA and only get to use 70%?



Rent's Rule

- T∞g^p
 - T = number of inputs and outputs
 - g = number of internal components
 - p typically between 0.5 (regular) and 0.8 (random)
- In a square, perimeter=4·area^{0.5}
 - unless regular, I/O signals grow faster than available routes exiting a design area
- Need hierarchy of progressively longer additional routing resources

long routes also reduce delay when going far

Virtex-II Routing Architecture


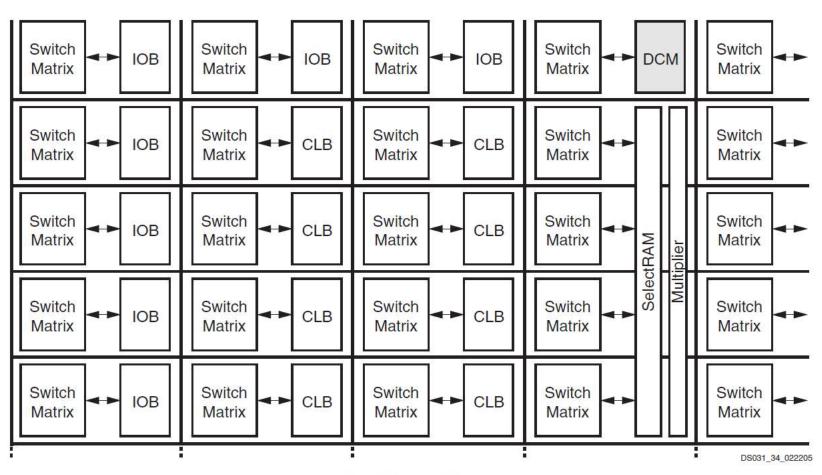


Figure 48: Routing Resources

[Figure 48: Virtex-II Platform FPGAs: Complete Data Sheet]

Virtex-II Routing Architecture

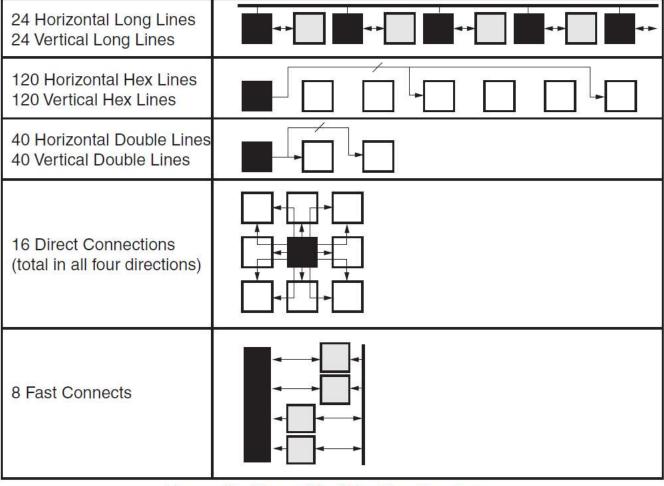

ater architectures extended n reach and in diagonals

Figure 49: Hierarchical Routing Resources


Separate, dedicated clock trees

[Figure 49: Virtex-II Platform FPGAs: Complete Data Sheet]

Between-Die Routing in 2.5D IC


Virtex7 Stacked Silicon Interconnect (SSI), 2011

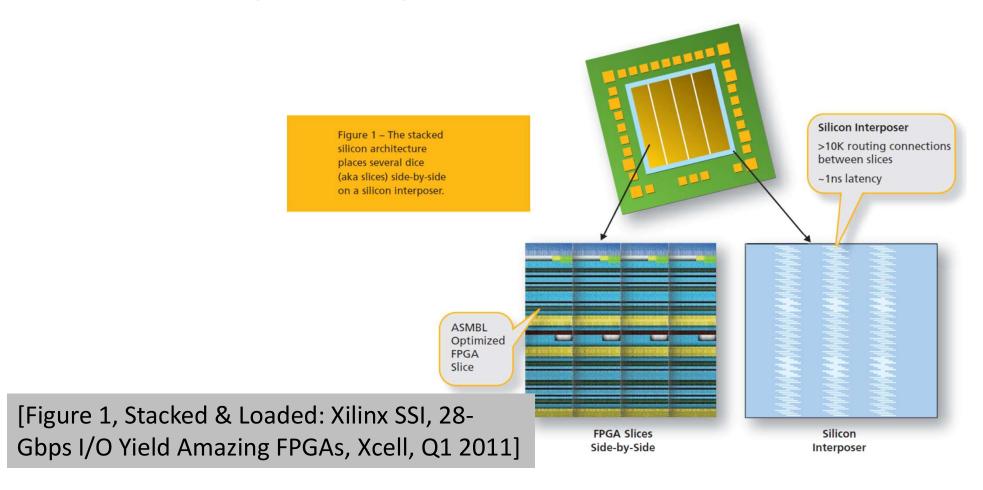- Longest routes go across dies carried on interposer
- No change to design tool and abstraction




Intel Stratix-X HyperFlex

- Long routes need buffered repeaters; very long routes need pipelining
- Add (bypassable) pipeline registers throughout
- RTL designs have to be pipelined explicitly to benefit; high-level synthesized designs leverage directly
- a high-freq strategy—
 e.g., 0.5xlogic at 2xfreq
 for perf. parity

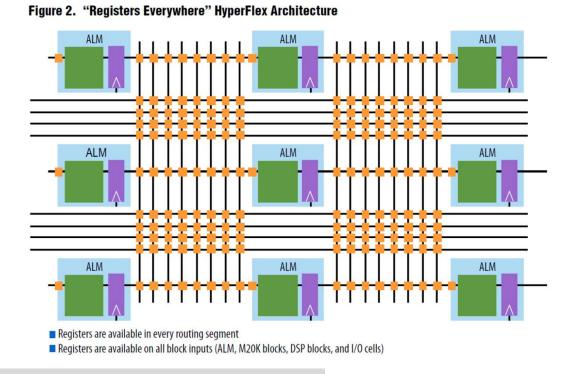

[Figure 2: Understanding How the New HyperFlex Architecture Enables Next-Generation High-Performance Systems]


Don't Forget Configurable I/O

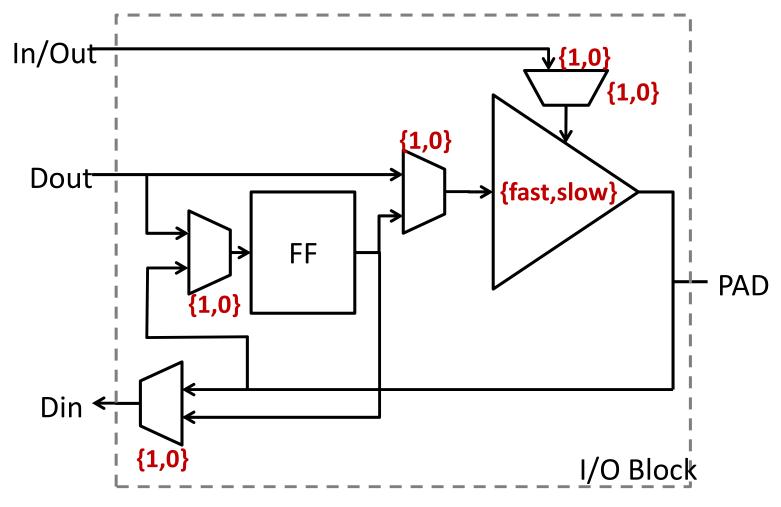

- real devices more complicated

- modern devices support special signaling and protocols

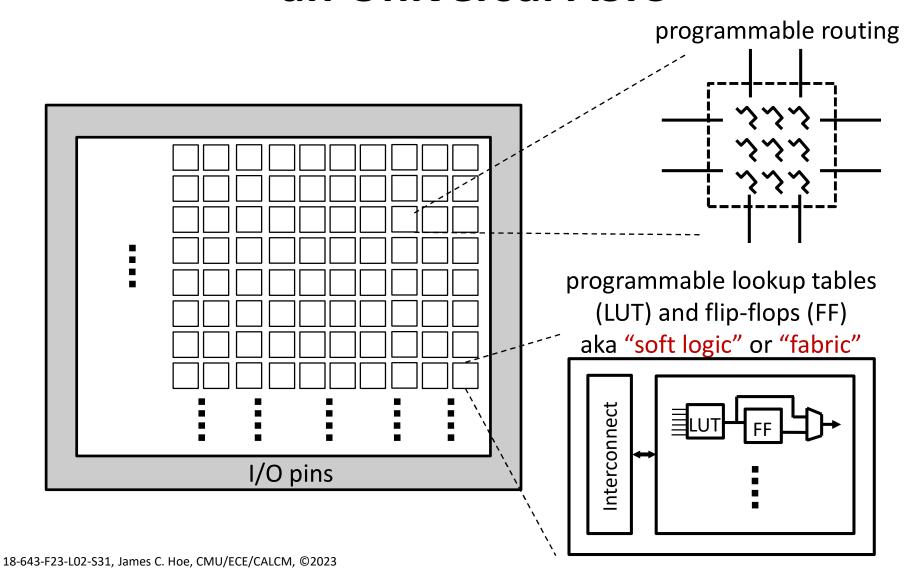Putting it all together: an Universal ASIC



Bitstream defines the chip

 After power up, SRAM FPGA loads bitstream from somewhere before becoming the "chip"

a bonus "feature" for sensitive devices that need to forget what it does

- Many built-in loading options
- Non-trivial amount of time; must control reset timing and sequence with the rest of the system
- Reverse-engineering concerns ameliorated by
 - encryption
 - proprietary knowledge

Return to this later in term

Parting Thoughts

- Birth of FPGAs rooted entirely in digital logic and ASIC concerns; today, you can use an FPGA without knowing any of this stuff
- You can find a lot of specific details on-line (databooks and research papers)
- So far still just the basic fabric
 - . . . more next time
 - saving "configuration" for later in term
 - won't say anything about low-level EDA